

Name: Kaustubh V. Mali

Roll No: 29

Assignment - 1

a) Interface 32K byte of EPROM Memory to 8086 Use full decoding

1. 32K byte:-

2. Ending address -  $ffffH$

Starting address - Ending Address - Memory span

- Ending Address - 32K.

-  $ffffH$  -  $7fffH$

-  $f8000H$

3. IC of 512 byte size for even and odd memory bank i.e 2 IC 27128 is required.

4. IC 27128 : 14 Address lines :  $A_0 - A_{13}$

8 Data lines :  $D_0 - D_7$

Memory Map Table

Memory chip

$A_{19} A_{18} A_{17} A_{16} A_{15} A_{14} A_{13} A_{12} A_{11} A_{10} A_9 A_8 A_7 A_6 A_5 A_4 A_3 A_2 A_1 A_0$

Even

EPROM

ODD

EPROM

Memory chip

Even


EPROM

ODD

EPROM

	$A_{19}$	$A_{18}$	$A_{17}$	$A_{16}$	$A_{15}$	$A_{14}$	$A_{13}$	$A_{12}$	$A_{11}$	$A_{10}$	$A_9$	$A_8$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$	Address
Even	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	$f8000H$
EPROM	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	$ffffH$
ODD	1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	$f8001H$
EPROM	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	$ffffH$

FOR EDUCATIONAL USE

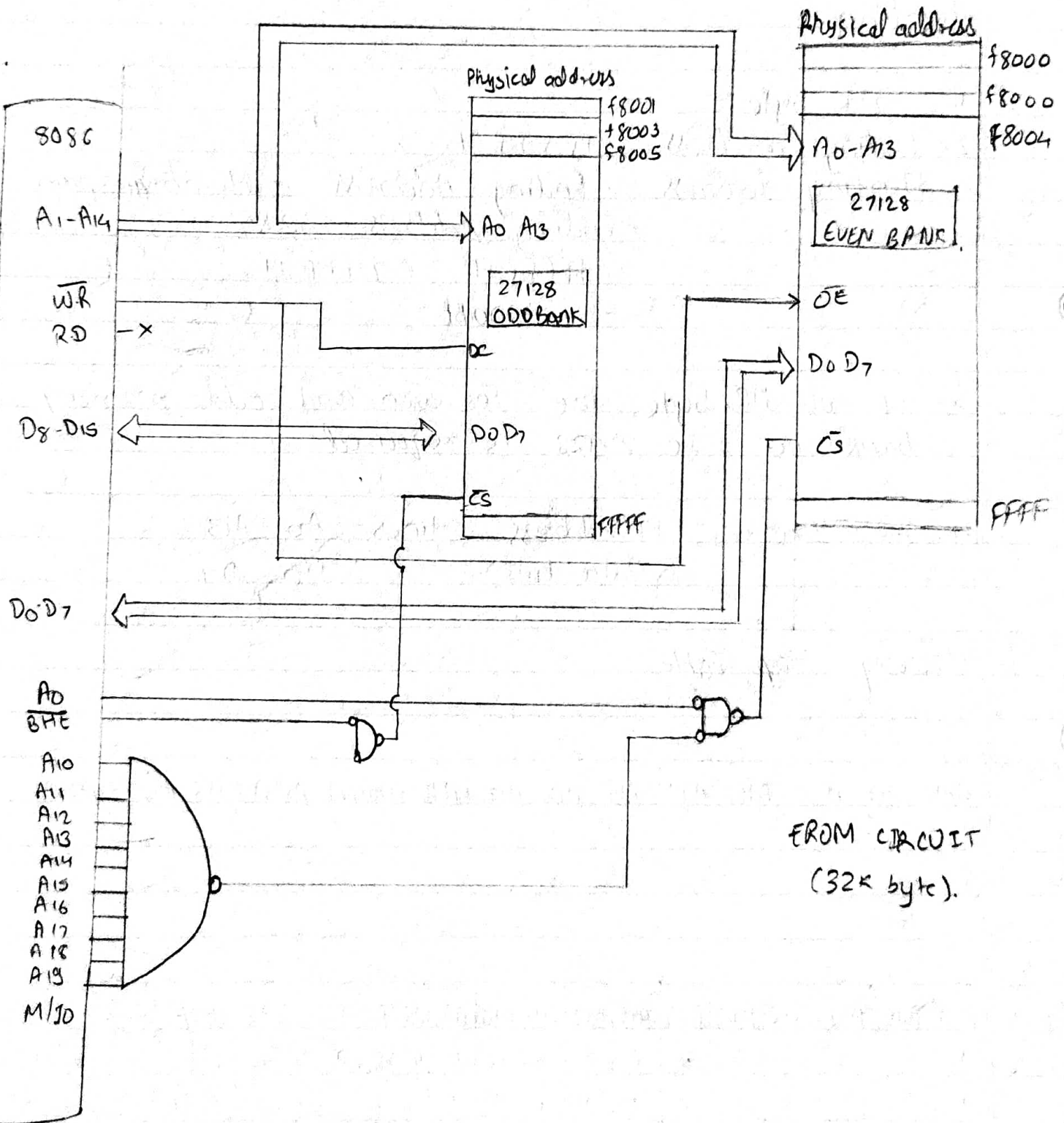

Kaustubh Mali

Roll No: 29

Assignment: 2

Q1/ Interface 13K byte of SRAM memory to 8086 with starting address 20000H. Use IC 6264. Use full decoding

1. 13K byte :  $13K \times 8$

2. Starting Address : D0000H

Ending address : Starting address + Memory Span

Starting address +  $13K \times 2$

D0000H + 16K

D0000H + 3FFF

: D3FFFH

3. 2 IC of  $13K \times 8$  for even and odd memory bank i.e. 2 IC of 6264

4. IC 6264 : 13 address line - A<sub>0</sub> - A<sub>12</sub>

8 data lines - D<sub>0</sub> - D<sub>7</sub>

Memory Map Table.

Memory Chip	A <sub>13</sub>	A <sub>16</sub>	A <sub>17</sub>	A <sub>16</sub>	A <sub>15</sub>	A <sub>14</sub>	A <sub>13</sub>	A <sub>12</sub>	A <sub>11</sub>	A <sub>10</sub>	A <sub>9</sub>	A <sub>8</sub>	A <sub>7</sub>	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	WE	Address
6264 EVEN RAM.	1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	D0000
	1	1	0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	0	1	D3FFE
6264 EVEN RAM	1	1	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	D0001
	1	1	0	1	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	0	D3FFF

